

Bridge of Wine — Solution

Y23 (2023) — English translation

A1

2.00 pts

Express the bridge balancing condition as a ratio only between the values of its elements. At what frequency f_{bal} does balancing occur?

Answer:

$$\frac{C_1}{C_2} = \frac{R_4}{R_3} - \frac{R_2}{R_1} f_{\text{bal}} = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

A2

4.00 pts

Using the Wien bridge, find the capacitances of the capacitors given to you as accurately as possible. Estimate the error of the received answers. Note: Since the “ground” of the generator and the oscilloscope are common, when connecting devices directly to the circuit, one of the Wien bridge components will actually be excluded from the circuit (its two terminals will have the same potential). To solve this problem you need to use a transformer. One of its windings must be connected to the Wien bridge, and data must be taken from the second winding on an oscilloscope. Note: Only plug the transformer into a small breadboard, since its legs can damage the contacts of a large one!

Note: Since the “ground” of the generator and the oscilloscope are common, when connecting devices directly to the circuit, one of the Wien bridge components will actually be excluded from the circuit (its two terminals will have the same potential). To solve this problem you need to use a transformer. One of its windings must be connected to the Wien bridge, and data must be taken from the second winding on an oscilloscope.

Note: Only plug the transformer into a small breadboard, since its legs can damage the contacts of a large one!

The resistor values are $1.00 \pm 0.01 \text{ k}\Omega \times 2$, $2.00 \pm 0.02 \text{ k}\Omega$ and $22.0 \pm 0.5 \text{ }\Omega$. To more accurately determine the capacities, it makes sense to increase the quotient $\frac{R_4}{R_3}$ and decrease $\frac{R_2}{R_1} \implies R_1 = 2 \text{ k}\Omega$, $R_2 = 22 \text{ }\Omega$, $R_3 = 1 \text{ k}\Omega$. Then the error of the term $\frac{R_2}{R_1}$ can actually be neglected. The Wien bridge, assembled in this way, allows you to measure the capacitance of capacitors 1 – 6. To measure the capacitance of capacitor 7, you can connect the remaining resistor $1 \text{ k}\Omega$ in series with the rheostat. The measurement results are shown in the table below. For more accurate measurement of small capacitances, you can use other bridge assemblies, for example, take $R_3 = 2 \text{ k}\Omega$.

Answer: Capacitor No. 1 2 3 4 5 6 7 Capacitance C , nF 102 148 208 302 424 664 954 Error ΔC , nF 3 4 6 11 14 19 26

B1

2.00 pts

Find the transfer function of the Wien bridge $H(f)$. At what frequency f_0 does this function have a singularity? To what value H_∞ does the transfer function reach in the limit of high and low frequencies?

Answer:

$$H(f) = \frac{1}{3} \frac{|1 - \Omega^2|}{\sqrt{(1 - \Omega^2)^2 + 9\Omega^2}}, \quad \Omega = 2\pi f R_1 C_1 f_0 = \frac{1}{2\pi R_1 C_1}, \quad H_\infty = \frac{1}{3}$$

B2

1.00 pts

Build a frequency filter from existing equipment. By applying a sinusoidal signal to the input, find the minimum experimentally achievable value of the transfer function $H_{\text{exp min}}$.

The only way to assemble the required bridge is to use $C_1 = C_0$ and a rheostat as R_3 and R_4 . It is worth noting that when minimizing the transfer function, the voltage on the oscilloscope will fluctuate at a frequency that is 2 times the input. Thus, the actual transfer function of a Wien bridge is limited by nonlinear effects.

Answer:

$$H_{\text{exp min}} = 0.02 \dots 0.03$$

B3

1.00 pts

Propose a method to filter out the DC component and the carrier harmonic of the diode signal and find the relative amplitude $\frac{U_{\text{high}}}{U_{\text{in}}}$ of the higher harmonics. Estimate the error using the result of the previous paragraph. Hint: You can assume that the transfer function of the Wien bridge reaches a constant fairly quickly. Please note that the transformer transfer function is not necessarily equal to 1!

Hint: You can assume that the transfer function of the Wien bridge reaches a constant fairly quickly. Please note that the transformer transfer function is not necessarily equal to 1!

By tuning the oscillator to frequency f_0 , we can filter out the carrier harmonic. The component constant disappears because a transformer is used to connect the oscilloscope. Let's measure the relative amplitude of the signal on an oscilloscope (the frequency of this signal should be equal to $2f_0$), $\frac{U_{\text{out}}}{U_{\text{in}}} \sim 0.08$. Let's measure the transfer function of the transformer at frequency f_0 by connecting it directly to the source. We get $H_{\text{trans}} \approx 0.5$. Transfer function of the Wien bridge according to condition $= 1/3$. Then

$$\frac{U_{\text{high}}}{U_{\text{in}}} = \frac{3}{H_{\text{trans}}} \frac{U_{\text{out}}}{U_{\text{in}}} \sim 0.5, \quad \Delta \left(\frac{U_{\text{high}}}{U_{\text{in}}} \right) = \frac{3H_{\text{exp min}}}{H_{\text{trans}}} \sim 0.1$$

Answer:

$$\frac{U_{\text{high}}}{U_{\text{in}}} = 0.5 \pm 0.1$$