

Topological insulator — Solution

Y26 (2026) — English translation

A1

0.40 pts


Using Kirchhoff's rules, obtain a system of equations relating V , u and q . Express your answer using V , u , q , L , C_1 , C_2 and ω .

Let us find the currents flowing in the links, knowing that at the point located to the right of the point C the potential is equal to ue^{iq} .

Now let's write the first Kirchhoff rule for nodes with potentials u and Ve^{iq} , respectively

$$\begin{cases} (V - u) \cdot i\omega C_1 = (u - Ve^{iq}) \cdot i\omega C_2 + \frac{u}{i\omega L}, \\ (u - Ve^{iq}) \cdot i\omega C_2 = e^{iq}(V - u) \cdot i\omega C_1 + \frac{Ve^{iq}}{i\omega L}. \end{cases}$$

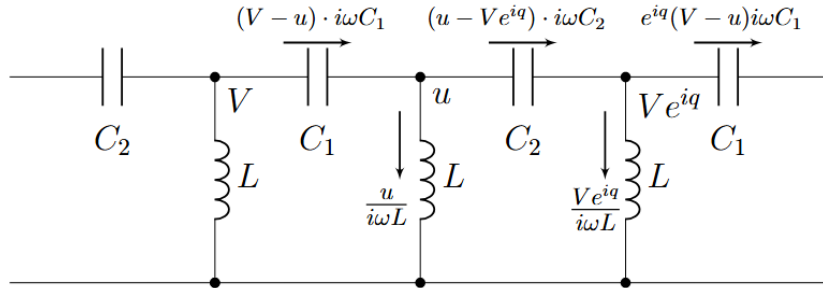The resulting system of equations is sufficient to obtain an expression for $\cos q(\omega)$.



A2

0.80 pts

From the resulting system, express $\cos q$ in terms of ω , L , C_1 and C_2 .

Method 1. From both equations we express $\frac{u}{V}$ and equate them. We obtain from equations 1 and 2, respectively:

$$\begin{cases} \frac{u}{V} = \frac{e^{iq} \cdot i\omega C_2 + i\omega C_1}{i\omega \cdot \left(C_1 + C_2 - \frac{1}{\omega^2 L} \right)}, \\ \frac{u}{V} = \frac{e^{iq} \cdot i\omega \cdot \left(C_1 + C_2 - \frac{1}{\omega^2 L} \right)}{e^{iq} \cdot i\omega C_1 + i\omega C_2}, \end{cases}$$

from which, equating $\frac{u}{V}$ from different equations to each other and reducing by $i\omega$, we obtain an equation containing only the unknown q :

$$(e^{iq}C_2 + C_1)(e^{iq}C_1 + C_2) = e^{iq} \left(C_1 + C_2 - \frac{1}{\omega^2 L} \right)^2.$$

Now we expand the bracket on the left and divide both sides of the equation on e^{iq} :

$$C_1^2 + C_2^2 + C_1C_2(e^{iq} + e^{-iq}) = \left(C_1 + C_2 - \frac{1}{\omega^2 L} \right)^2.$$

Taking into account that $e^{iq} + e^{-iq} = 2 \cos(q)$, obtain relation on $\cos q$

$$\cos q = \frac{\left(C_1 + C_2 - \frac{1}{\omega^2 L}\right)^2 - C_1^2 - C_2^2}{2 \cdot C_1 C_2}.$$

Method 2. In fact, it is faster to proceed somewhat differently. Write the system of equations as linear relations in V and u :

$$\begin{cases} V (C_1 + C_2 e^{iq}) + u \left(-C_1 - C_2 + \frac{1}{\omega^2 L}\right) = 0, \\ V \left(-C_1 - C_2 + \frac{1}{\omega^2 L}\right) + u (C_1 + C_2 e^{-iq}) = 0. \end{cases}$$

For the system has a non-trivial solution (an infinite number of them), it is necessary and sufficient to set the principal determinant of the system to zero. Thus,

$$(C_1 + C_2 e^{iq}) (C_1 + C_2 e^{-iq}) = \left(C_1 + C_2 - \frac{1}{\omega^2 L}\right)^2.$$

Finally,

$$\cos q = \frac{\left(C_1 + C_2 - \frac{1}{\omega^2 L}\right)^2 - C_1^2 - C_2^2}{2 \cdot C_1 C_2}.$$

Now let's open the parentheses on the left and divide both sides of the equation by e^{iq} :

$$C_1^2 + C_2^2 + C_1 C_2 (e^{iq} + e^{-iq}) = \left(C_1 + C_2 - \frac{1}{\omega^2 L}\right)^2.$$

Considering that $e^{iq} + e^{-iq} = 2 \cos(q)$, we obtain the relation for $\cos q$

$$\cos q = \frac{\left(C_1 + C_2 - \frac{1}{\omega^2 L}\right)^2 - C_1^2 - C_2^2}{2 \cdot C_1 C_2}.$$

Method 2. In fact, it's faster to do things a little differently. Let us write the system of equations as linear with respect to V and u ,

$$\begin{cases} V (C_1 + C_2 e^{iq}) + u \left(-C_1 - C_2 + \frac{1}{\omega^2 L}\right) = 0, \\ V \left(-C_1 - C_2 + \frac{1}{\omega^2 L}\right) + u (C_1 + C_2 e^{-iq}) = 0. \end{cases}$$

For a system to have a nontrivial solution (there are an infinite number of them), it is necessary and sufficient to set the main determinant of the system equal to zero. Thus,

$$(C_1 + C_2 e^{iq}) (C_1 + C_2 e^{-iq}) = \left(C_1 + C_2 - \frac{1}{\omega^2 L}\right)^2.$$

Finally,

$$\cos q = \frac{\left(C_1 + C_2 - \frac{1}{\omega^2 L}\right)^2 - C_1^2 - C_2^2}{2 \cdot C_1 C_2}.$$

A3

0.60 pts

Determine at what frequencies the wave vector q will have an imaginary part. Express your answer in terms of L , C_1 and C_2 .

First way. Let us give an expression for $\cos q$

$$\cos q = 1 - \frac{C_1 + C_2}{C_1 C_2} \cdot \frac{1}{\omega^2 L} + \frac{1}{2C_1 C_2} \cdot \left(\frac{1}{\omega^2 L} \right)^2$$

Solve two square inequality

$$\begin{aligned} \cos q &> 1; \\ -\frac{C_1 + C_2}{C_1 C_2} \cdot \frac{1}{\omega^2 L} + \frac{1}{2C_1 C_2} \cdot \left(\frac{1}{\omega^2 L} \right)^2 &> 0; \\ \frac{1}{\omega^2 L} \left(\frac{1}{\omega^2 L} - 2(C_1 + C_2) \right) &> 0; \\ \frac{1}{\omega^2 L} &\in (-\infty; 0) \cup (2(C_1 + C_2); +\infty); \\ \omega^2 L &\in \left(0; \frac{1}{2(C_1 + C_2)} \right) \end{aligned}$$

$$\begin{aligned} \cos q &< -1; \\ 2 - \frac{C_1 + C_2}{C_1 C_2} \cdot \frac{1}{\omega^2 L} + \frac{1}{2C_1 C_2} \cdot \left(\frac{1}{\omega^2 L} \right)^2 &< 0; \\ \left(\frac{1}{\omega^2 L} \right)^2 - 2(C_1 + C_2) \cdot \frac{1}{\omega^2 L} + 4C_1 C_2 &< 0; \\ \left(\frac{1}{\omega^2 L} - 2C_1 \right) \left(\frac{1}{\omega^2 L} - 2C_2 \right) &< 0; \\ \frac{1}{\omega^2 L} &\in (2C_1; 2C_2); \\ \omega^2 L &\in \left(\frac{1}{2C_1}; \frac{1}{2C_2} \right) \end{aligned}$$

From the union of the systems of inequalities we obtain the final answer

$$\omega \in \left[0; \frac{1}{\sqrt{2(C_1 + C_2)L}} \right) \cup \left(\frac{1}{\sqrt{2C_2L}}; \frac{1}{\sqrt{2C_1L}} \right).$$

$$\cos q = 1 - \frac{C_1 + C_2}{C_1 C_2} \cdot \frac{1}{\omega^2 L} + \frac{1}{2C_1 C_2} \cdot \left(\frac{1}{\omega^2 L} \right)^2$$

Let's solve two quadratic inequalities

From combining the system of inequalities we obtain the final answer

$$\omega \in \left[0; \frac{1}{\sqrt{2(C_1 + C_2)L}} \right) \cup \left(\frac{1}{\sqrt{2C_2L}}; \frac{1}{\sqrt{2C_1L}} \right).$$

Second way. Let's write down the expression for $x = \cos q$

$$x = 1 - \frac{C_1 + C_2}{C_1 C_2} \cdot \frac{1}{\omega^2 L} + \frac{1}{2C_1 C_2} \cdot \frac{1}{\omega^4 L^2}.$$

Obtain, that dependence $x(\frac{1}{\omega^2 L})$ quadratic, construct it graph qualitative graph, on which note point intersection with straight $\cos q = 1$ and $\cos q = -1$.

The resulting graph can be qualitatively reconstructed in the $y = \cos q$ $x = \omega^2 L$ axes, preserving all extrema and transforming the x axis.

Let us introduce the notation corresponding to the coordinates x at the point of intersection of the constructed graph with the lines $\cos q = 1$, $\cos q = -1$. At the point of intersection of the graph with $\cos q = 1$, $\omega = \omega_1$. At the intersection point of the graph with $\cos q = -1$, $\omega = \omega_2$ and $\omega = \omega_3$. Let's compose and solve quadratic equations for $\frac{1}{\omega^2 L}$

$$\begin{aligned}\cos q &= 1; \\ -\frac{C_1 + C_2}{C_1 C_2} \cdot \frac{1}{\omega^2 L} + \frac{1}{2C_1 C_2} \cdot \left(\frac{1}{\omega^2 L}\right)^2 &= 0; \\ \frac{1}{\omega^2 L} \left(\frac{1}{\omega^2 L} - 2(C_1 + C_2)\right) &= 0; \\ \frac{1}{\omega^2 L} &= 2(C_1 + C_2) \text{ or } \frac{1}{\omega^2 L} = 0\end{aligned}$$



$$\begin{aligned}\cos q &= -1; \\ 2 - \frac{C_1 + C_2}{C_1 C_2} \cdot \frac{1}{\omega^2 L} + \frac{1}{2C_1 C_2} \cdot \left(\frac{1}{\omega^2 L}\right)^2 &= 0; \\ \left(\frac{1}{\omega^2 L}\right)^2 - 2(C_1 + C_2) \cdot \frac{1}{\omega^2 L} + 4C_1 C_2 &= 0; \\ \left(\frac{1}{\omega^2 L} - 2C_1\right) \left(\frac{1}{\omega^2 L} - 2C_2\right) &= 0; \\ \frac{1}{\omega^2 L} &= 2C_1 \text{ or } \frac{1}{\omega^2 L} = 2C_2\end{aligned}$$

Comparing the solutions of the equations with the graph, we get the answer

$$\omega \in \left[0; \frac{1}{\sqrt{2(C_1 + C_2)L}}\right) \cup \left(\frac{1}{\sqrt{2C_2L}}; \frac{1}{\sqrt{2C_1L}}\right).$$

Comparing the solutions of the equations with the graph, we get the answer
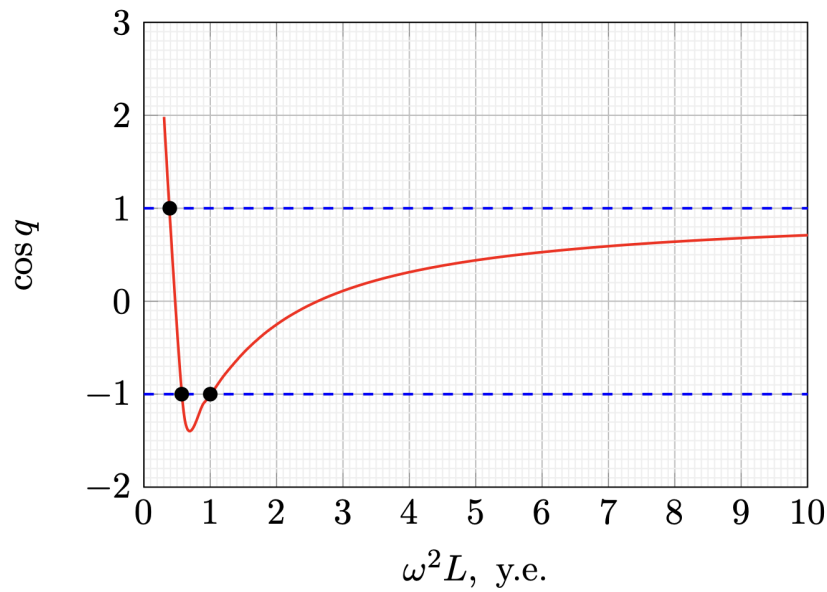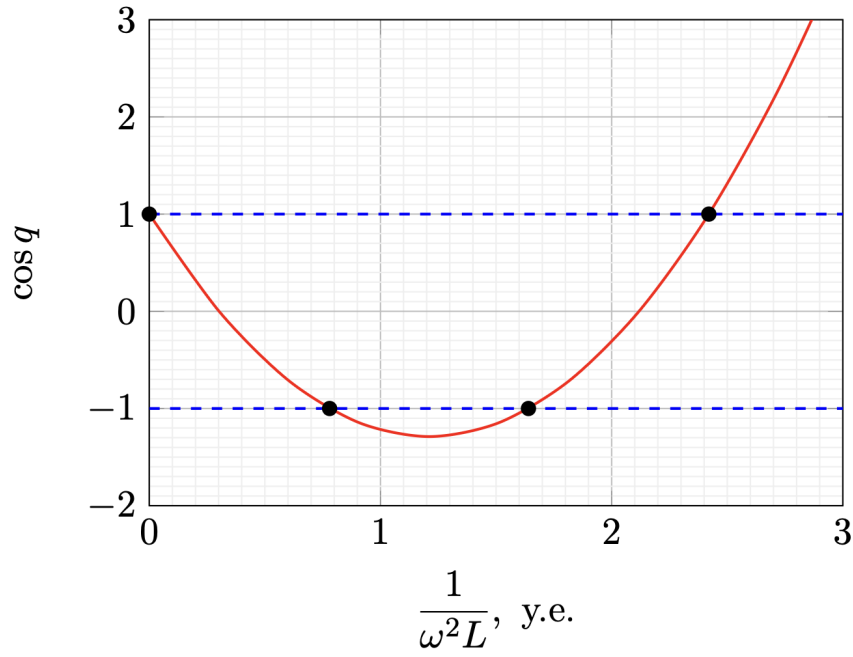
$$\omega \in \left[0; \frac{1}{\sqrt{2(C_1 + C_2)L}}\right) \cup \left(\frac{1}{\sqrt{2C_2L}}; \frac{1}{\sqrt{2C_1L}}\right).$$



A4

1.50 pts

Measure the dependence of the real and imaginary components of the wave vector $\Re(q)$ and $\Im(q)$ on the frequency f . Describe the measurement technique. Take measurements in the frequency range from 650 kHz to 1300 kHz in steps of 50 kHz. For each frequency f , the value of both $\Re(q)$ and $\Im(q)$ must be obtained.

Let's connect the generator to the circuit according to the instructions in the condition. Using two oscilloscope channels, we will measure the doubled voltage amplitude on the generator U_0 and the doubled voltage amplitude on the first link U_1 . Using the phase shift of the signals on an oscilloscope we will measure $\Re(q)$

$$\Re(q) = 2\pi f \Delta T$$

From the ratio of amplitudes of the signals we measure $\Im(q)$

$$\Im(q) = \ln \frac{U_0}{U_1}$$

Note. For measurements in the frequency range $f \in [770; 890]$ kHz the chain is in the conducting state (correspond range frequency $f \in \left(\frac{1}{\sqrt{2(C_1 + C_2)L}}; \frac{1}{\sqrt{2C_2L}} \right)$), therefore, during measurements, the influence of the reflected wave can be noticed. When linearized, these points will produce outliers.

Using the phase shift of the signals on an oscilloscope we will measure $\Re(q)$

$$\Re(q) = 2\pi f \Delta T$$

Based on the ratio of the amplitudes on the signals, we will measure $\Im(q)$

$$\Im(q) = \ln \frac{U_0}{U_1}$$

Note. When making measurements in the frequency range $f \in [770; 890]$ kHz, the circuit is in a conducting state (corresponding to the frequency range $f \in \left(\frac{1}{\sqrt{2(C_1 + C_2)L}}; \frac{1}{\sqrt{2C_2L}} \right)$), so during measurements you can notice the influence of the reflected wave. When linearized, these points will produce outliers.

f , kHz	ΔT , ns	U_0 , mV	U_1 , mV	$\Re(q)$	$\Im(q)$	f^{-2} , 10^{-12} s ²	$\Re(\cos q)$	$(1 - \cos q) \cdot f^2$, 10^{12} Hz ²
650	0	57.6	8	0.00	-1.97	2.37	3.67	-1.13
700	32	128	34.4	0.14	-1.31	2.04	1.98	-0.48
750	216	284	408	1.02	0.36	1.78	0.56	0.25
800	452	616	416	2.27	-0.39	1.56	-0.70	1.09
850	396	328	172	2.11	-0.65	1.38	-0.63	1.18
900	480	304	212	2.71	-0.36	1.23	-0.97	1.60
950	516	252	134	3.08	-0.63	1.11	-1.21	1.99
1000	496	232	112	3.12	-0.73	1.00	-1.28	2.28
1050	484	232	110	3.19	-0.75	0.91	-1.29	2.53
1100	460	244	120	3.18	-0.71	0.83	-1.26	2.74
1150	436	268	142	3.15	-0.64	0.76	-1.21	2.92
1200	416	304	182	3.14	-0.51	0.69	-1.13	3.07
1250	396	368	264	3.11	-0.33	0.64	-1.06	3.21
1300	388	520	464	3.17	-0.11	0.59	-1.01	3.39

A5

1.00 pts

Linearize the dependence of $\Re(\cos q)$ on the frequency of the generator f and determine the coefficients of the linear dependence.

Using the result of the previous points

$$\cos q = 1 - \frac{C_1 + C_2}{C_1 C_2} \cdot \frac{1}{\omega^2 L} + \frac{1}{2C_1 C_2} \cdot \frac{1}{\omega^4 L^2}.$$


Transforming the expression we obtain a linearization $(1 - \cos q) \cdot \omega^2 L$ from $\frac{1}{\omega^2 L}$

$$(1 - \cos q) \cdot \omega^2 L = \frac{C_1 + C_2}{C_1 C_2} - \frac{1}{2C_1 C_2} \cdot \frac{1}{\omega^2 L}.$$

We linearize the dependence and construct a graph.

Linear dependence parameters (slope coefficient and shift index, respectively)
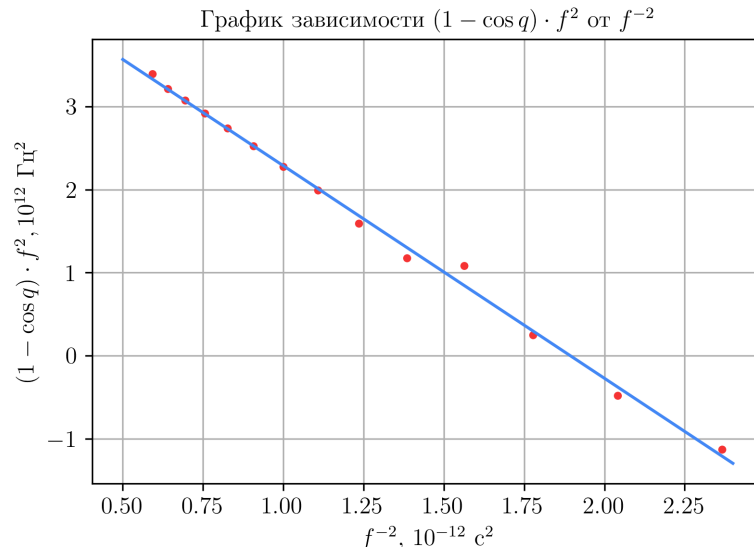
$$k = -2.58 \cdot 10^{24} \text{ Hz}^4, \quad b = 4.86 \cdot 10^{12} \text{ Hz}^2.$$



A6

0.70 pts

Using the coefficients found in A5, determine the capacitances of capacitors C_1 and C_2 ($C_1 < C_2$).

According to the theory,

$$k = -\frac{(2\pi)^2}{2L^2} \cdot \frac{1}{C_1 C_2}, \quad b = \frac{(2\pi)^2}{L} \cdot \frac{C_1 + C_2}{C_1 C_2}.$$

From where we get (using, for example, Vieta's theorem for a quadratic equation whose roots are inverse capacitances)

$$\begin{aligned} C_1 &= 0.43 \text{ nF}, \\ C_2 &= 0.89 \text{ nF}. \end{aligned}$$

$$k = -\frac{(2\pi)^2}{2L^2} \cdot \frac{1}{C_1 C_2}, \quad b = \frac{(2\pi)^2}{L} \cdot \frac{C_1 + C_2}{C_1 C_2}.$$

Where do we get it from (using, for example, Vieta's theorem for a quadratic equation whose roots are inverse capacities)

$$\begin{aligned} C_1 &= 0.43 \text{ nF}, \\ C_2 &= 0.89 \text{ nF}. \end{aligned}$$

B1

0.80 pts

Express the impedances z_r and z_l for waves traveling to the right and left. Express your answer in terms of C_1 , C_2 , L , q and ω .

Let's arrange the currents and potentials in the circuit similarly to part A

Then we write down the wave impedance z_r for a wave traveling to the right


$$z_r = \frac{V}{I} = \frac{V}{V - u} \cdot \frac{1}{i\omega C_1}.$$

Substitute relation for $\frac{u}{V}$, obtain in part A

$$z_r = \frac{1}{1 - \frac{C_1 + C_2 e^{iq}}{C_1 + C_2 - \frac{1}{\omega^2 L}}} \cdot \frac{1}{i\omega C_1} = \frac{C_1 + C_2 - \frac{1}{\omega^2 L}}{C_2(1 - e^{iq}) - \frac{1}{\omega^2 L}} \cdot \frac{1}{i\omega C_1}.$$

The expression for z_l can be obtained by the substitution $q \rightarrow -q$
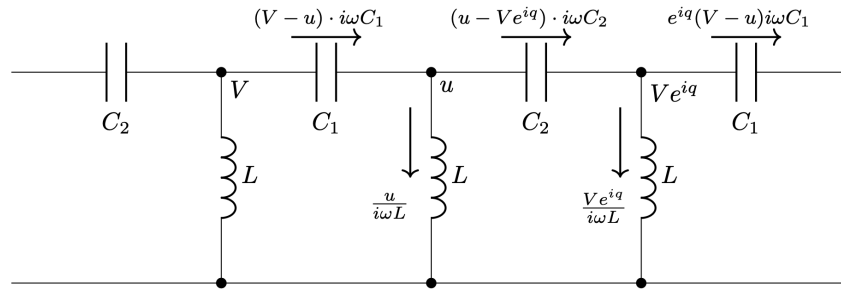
$$z_l = \frac{C_1 + C_2 - \frac{1}{\omega^2 L}}{C_2(1 - e^{-iq}) - \frac{1}{\omega^2 L}} \cdot \frac{1}{i\omega C_1}.$$



B2

0.60 pts

Write down the boundary condition connecting the complex stress amplitudes $V_r(0, t)$ and $V_l(0, t)$. The answer will be an equation containing $V_r(0, t)$, $V_l(0, t)$, z_r , z_l , q and N .

Let's write the boundary condition for the current flowing from a link in the circuit with number N

$$I_r(N, t) + I_l(N, t) = 0.$$

Let's express the currents of each of the waves through the corresponding voltages on the zero link

$$\frac{V_r(0, t) e^{iqN}}{z_r} + \frac{V_l(0, t) e^{-iqN}}{z_l} = 0,$$

$$V_l(0, t) = -\frac{z_l}{z_r} V_r(0, t) e^{2iqN}.$$

B3

1.20 pts

Obtain an expression for the total impedance modulus of a circuit $|z|$ consisting of N links. Express your answer using N , q and $|z_r|$.

Let's write an expression for the total impedance of the circuit by substituting the amplitude of voltage and current as the sum of the amplitudes of voltage and current of two waves

$$z = \frac{V_r(0, t) + V_l(0, t)}{I_r(0, t) + I_l(0, t)} = \frac{V_r(0, t) + V_l(0, t)}{\frac{V_r(0, t)}{z_r} + \frac{V_l(0, t)}{z_l}}.$$

Substitute obtain relation on amplitude voltage wave

$$z = \frac{1 - \frac{z_l}{z_r} e^{2iqN}}{\frac{1}{z_r} + \frac{1}{z_l} \left(-\frac{z_l}{z_r} e^{2iqN} \right)} = \frac{z_r - z_l e^{2iqN}}{1 - e^{2iqN}}.$$

Substitute relation on impedance and neglect $\frac{1}{\omega^2 L}$

$$z = z_r \frac{1 - \frac{C_2(1 - e^{iq}) - \frac{1}{\omega^2 L}}{C_2(1 - e^{-iq}) - \frac{1}{\omega^2 L}} \cdot e^{2iqN}}{1 - e^{2iqN}} = z_r \frac{1 - \frac{1 - e^{iq}}{1 - e^{-iq}} \cdot e^{2iqN}}{1 - e^{2iqN}} = z_r \frac{1 + e^{2iq(N + \frac{1}{2})}}{1 - e^{2iqN}}.$$

Take magnitude/modulus from obtain expression

$$|z| = |z_r| \frac{\cos(q(N + \frac{1}{2}))}{\sin(qN)}.$$

B4

0.60 pts

Using the results obtained in Part A, write an equation for the frequencies at which the maximum impedance is achieved. Express your answer in terms of N , C_1 , C_2 , L , ω and the integer parameter m .

The maximum modulus is reached at $qN = \pi\Delta n$. Let us obtain an expression for the frequencies at which the impedance extrema

$$\arccos\left(\frac{1}{2C_1C_2}\left(\frac{1}{\omega^2L} - (C_1 + C_2)\right)^2 - (C_1^2 + C_2^2)\right) = \frac{\pi\Delta n}{N}.$$

are reached

B5

1.00 pts

Measure the frequencies at which the maximum impedance modulus is realized. Measurements should be carried out at frequencies $1400 \text{ kHz} < f < 6000 \text{ kHz}$, at which the LC circuit passes into the conduction band.

Let's connect to the board according to the condition, we will measure the frequencies at which the minimum amplitude of the voltage across the resistor is achieved. We obtain the signal on the resistor using the math oscilloscope mode, subtracting from the signal taken from the generator the signal taken on the J2 - GND contacts.

$n \text{ } f_{rez}, \text{ kHz}$

1	1466	3.49	2	1590	3.70	3	1717	3.88	4	1920	4.10	5	2137	4.29	6	2489	4.52	7	2899	4.70	8	3579	4.90	9	4549	5.06
---	------	------	---	------	------	---	------	------	---	------	------	---	------	------	---	------	------	---	------	------	---	------	------	---	------	------

B6

0.80 pts

Linearize the relationship measured in step B5 and construct a linearized graph from which determine the number of links in the chain N .

Let us construct the dependence of $q = 2\pi - \arccos\left(\frac{1}{2C_1C_2}\left(\frac{1}{\omega^2L} - (C_1 + C_2)\right)^2 - (C_1^2 + C_2^2)\right)$ on n .

The slope is equal to $k = 0.198$, hence $N = 15.9 \approx 16$.

