

Maximum on capacitor

Y14 (2014) — English translation

The circuit, consisting of two capacitors with capacitance C_1 , C_2 and a coil with inductance L , is initially open. Capacitor C_1 is charged to a potential difference V , and capacitor C_2 remains uncharged.

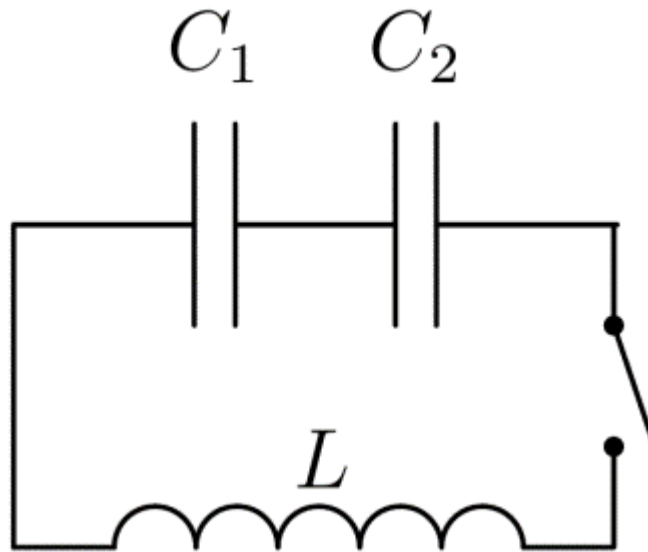


Fig. 1.

A1 Determine the maximum current in the circuit and the maximum voltage on the capacitor C_2 **3.00**
after closing the key.

Source: <https://pho.rs/p/3986>