

Maximum on capacitor

Y14 (2014) — English translation

The circuit, consisting of two capacitors with capacitance C_1 , C_2 and a coil with inductance L , is initially open. Capacitor C_1 is charged to a potential difference V , and capacitor C_2 remains uncharged.

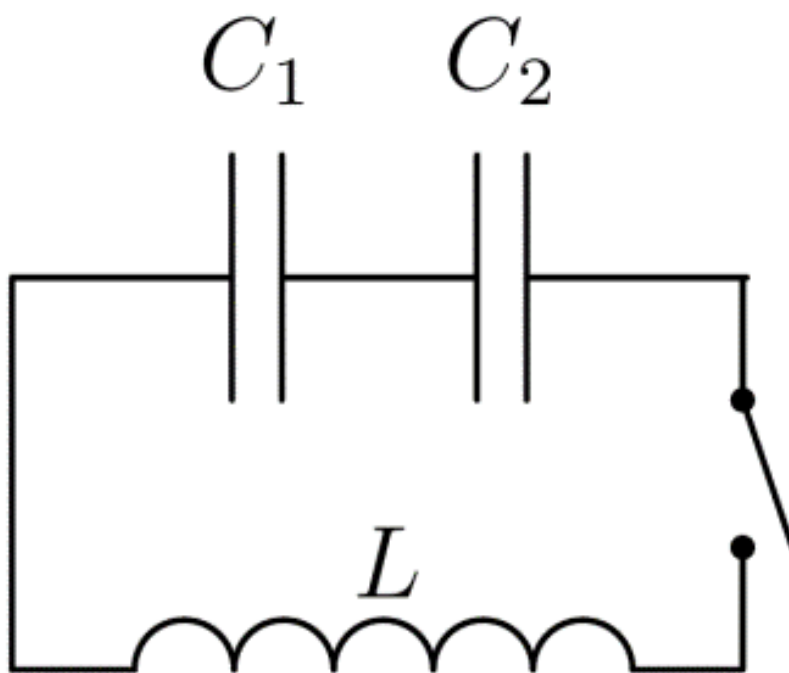


Figure 1: Figure 1.

A1	Determine the maximum current in the circuit and the maximum voltage on the capacitor C_2 after closing the key.	3.00
-----------	--	-------------

Source: <https://pho.rs/p/3986>