

Chain with coil

Y14 (2014) — English translation

There was no current in the circuit shown in the figure before the key was closed. The parameters of the elements are given.

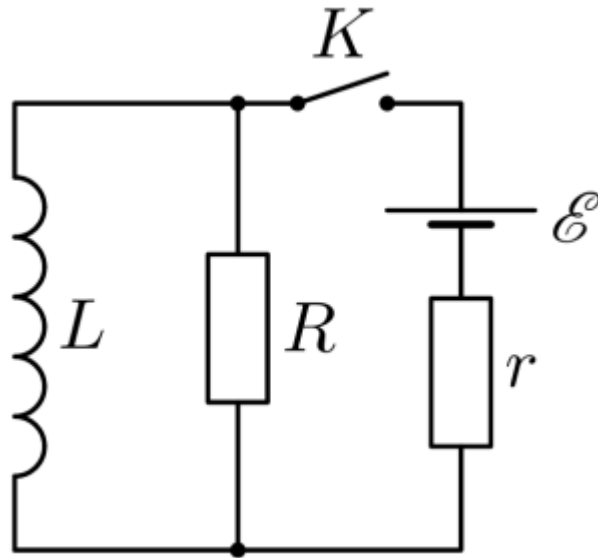


Fig. 1.

A1	What charge will flow through resistor R after the key is closed?	2.00
A2	How much heat will be released in resistor R after the switch is closed?	2.00

Source: <https://pho.rs/p/3987>