

Chain with coil

Y14 (2014) — English translation

There was no current in the circuit shown in the figure before the key was closed. The parameters of the elements are given.

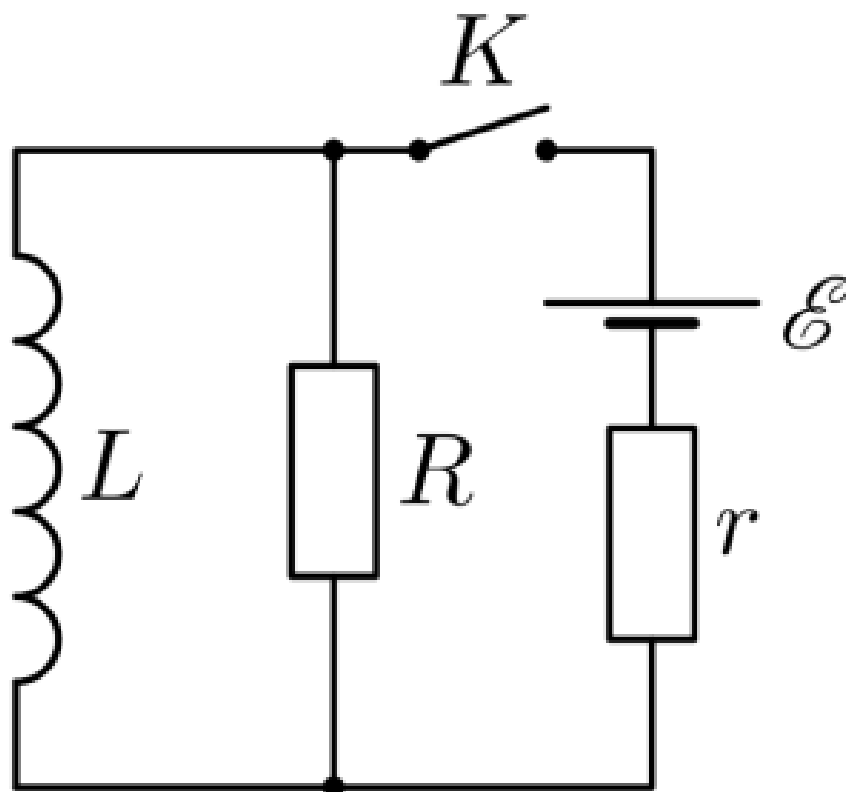


Figure 1: Figure 1.

A1	What charge will flow through resistor R after the key is closed?	2.00
A2	How much heat will be released in resistor R after the switch is closed?	2.00

Source: <https://pho.rs/p/3987>