

”Uncomplicated” capacitor

W22 (2022) — English translation

Part A. Charged plate in a capacitor.

In the middle between the identical uncharged metal plates of a flat capacitor with an area S and a distance between them $d \ll \sqrt{S}$ there is a dielectric plate of mass m of the same shape, charged uniformly over the surface with a charge $q > 0$. The capacitor plates were connected to a constant voltage source $\mathcal{E}$ with zero internal resistance. Then the plate is released. When moving, the capacitor plates remain motionless. Let us denote by x the deviation of the plate from the initial position, by q_1 the charge of the left plate, and by q_2 the charge of the right plate.

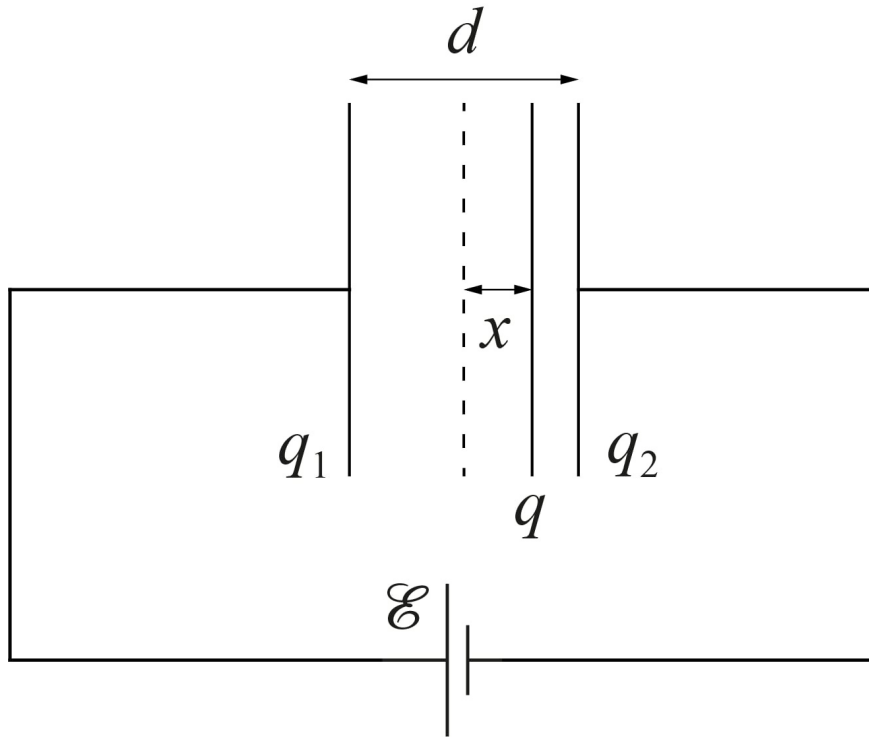


Figure 1: Figure 1.

A1 Express the charges of the capacitor plates $q_1(x)$ and $q_2(x)$ in terms of $\mathcal{E}$, S , d , q , x and physical constants. **0.50**

A2 Express the force of electrostatic interaction $F(x)$ of the plate with the plates in terms of $\mathcal{E}$, S , d , q , x and physical constants. **0.50**

It can be shown that the dependence of the displacement of the plate $x(t)$ on time has the following form

$$x(t) = Ae^{at} + Be^{-at} + C,$$

where a depends only on $\mathcal{E}$, S , d , q and m , while A , B and C are determined by the initial conditions.

A3	Express a , A , B and C in terms of $\mathcal{E}$, S , d , q , m and physical constants.	1.00
-----------	---	-------------

A4	Express the speed of the plate v^* at the moment of impact on the capacitor plate in terms of $\mathcal{E}$, S , d , q , m and physical constants.	1.00
-----------	---	-------------

Part B. Capacitor with Dielectric

A flat capacitor with plate area S and distance between them $d \ll \sqrt{S}$ is filled with a dielectric with dielectric constant ε and resistivity ρ . The dielectric and the plates have good electrical contact. Let the potential difference between the plates of the capacitor be V .

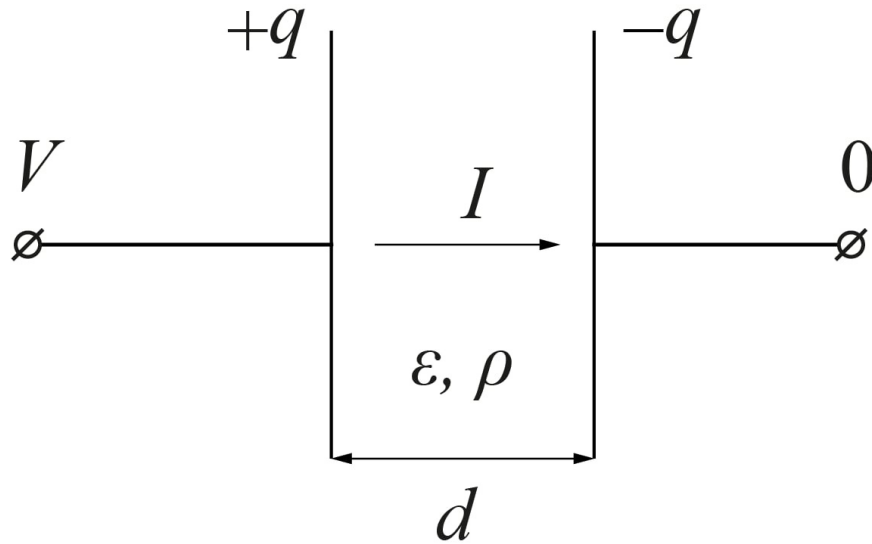


Figure 2: Figure 2.

B1	Find the charges q on the metal plates of the capacitor. Express your answer in terms of V , S , d , ε and physical constants.	0.30
-----------	--	-------------

B2	Find the current I flowing through the dielectric. Express your answer in terms of V , S , d , ρ and physical constants.	0.30
-----------	---	-------------

From the two previous points it follows that the circuit of such a capacitor in an electrical circuit is equivalent to some connection of a resistor with resistance R and a capacitor with capacitance C .

B3	Find R and C , and also indicate the type of connection of these elements (series or parallel).	0.40
-----------	---	-------------

Now the complex capacitor is connected to a constant voltage source $\mathcal{E}$, which has an internal resistance r . At the initial moment of time, the capacitor is not charged.

- B4** Find the time dependence of the current $I(t)$ flowing through the source. **2.00**
Express your answer in terms of $\mathcal{E}$, r , R , C and t .

Part C. Two-Dielectric Capacitor

A flat capacitor with a distance between plates d is filled with two dielectrics. One with dielectric constant ε_1 , resistivity ρ_1 and contact area with plates S_1 , and the other with dielectric constant ε_2 , resistivity ρ_2 and contact area with plates S_2 . Both dielectrics have good electrical contact with the capacitor plates.

- C1** Find the equivalent capacitance C_0 of this capacitor. Express your answer in **0.40**
terms of S_1 , S_2 , ε_1 , ε_2 , d and physical constants.

- C2** Find the equivalent resistance R_0 of this capacitor. Express your answer in **0.40**
terms of S_1 , S_2 , ρ_1 , ρ_2 and d .

This capacitor in series with the capacitor C is connected to a constant voltage source $\mathcal{E}$, which has zero internal resistance. While the key was open, the capacitors were not charged. The voltage across a complex capacitor is measured with an ideal voltmeter V .

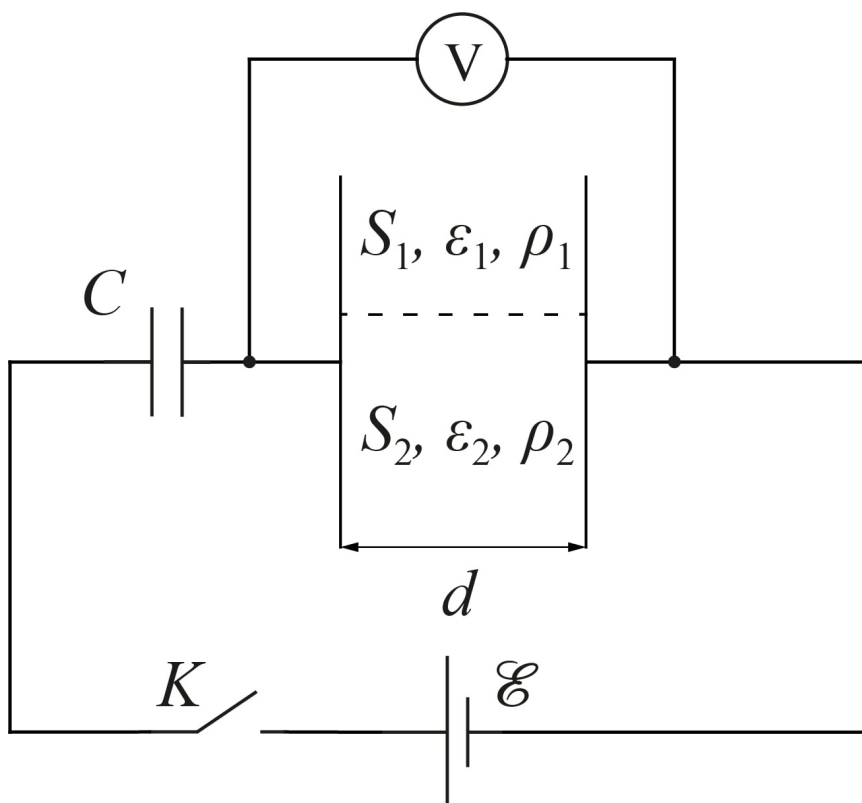


Figure 3: Figure 3.

- C3** Find the charge $q_C(0)$ on the capacitor capacitance C immediately after closing the switch. Express your answer using $\mathcal{E}$, C and C_0 . **0.40**

C4	Find the dependence of the voltmeter readings $V(t)$ on time t after closing the key. Express your answer in terms of $\mathcal{E}$, C , C_0 , R_0 and t .	1.30
-----------	---	-------------

C5	How much heat Q_{R_0} will be released at resistance R_0 ? Express your answer using $\mathcal{E}$, C and C_0 .	0.50
-----------	--	-------------

Useful integrals:

$$\int \frac{dx}{ax+b} = \frac{1}{a} \ln(ax+b) + C, \quad \int e^{ax} dx = \frac{e^{ax}}{a} + C.$$

Source: <https://pho.rs/p/271>